



ZIMBABWE EZEKIEL GUTI UNIVERSITY

FACULTY OF HEALTH, SCIENCE AND TECHNOLOGY

DEPARTMENT OF DIGITAL TECHNOLOGY

EXAMINATION PAPER

COURSE CODE	:	CDT115
COURSE TITLE	:	ELECTRONICS II
SPECIAL REQUIREMENTS	:	None
DURATION	:	3 Hours
LEVEL	:	1.2
DATE	:	2021

INSTRUCTIONS TO CANDIDATES:

1. Answer all questions.
2. Calculators and slide rules are allowed.
3. Show all the working.

Question 1

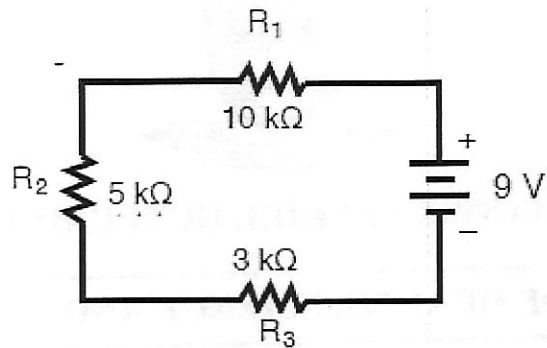


Figure 1

- What do you understand by elements in series? [2]
- What is the total resistance in the above circuit in figure 1? [3]
- What is the current in the circuit? [2]
- What is voltage drop through resistor R_1 ? [3]

Question 2

Compare and contrast DRAM and SRAM [10]

Question 3

- What is a transistor, where is its name derived from? [4]
- By means of diagrams explain the differences and the similarities between the *npn* and *pnp* transistors, mention both the minority and the majority carriers. [6]

Question 4

- Describe the common emitter connection. [4]
- Calculate I_E in a transistor for which $\beta = 40$ and $I_B = 20\mu\text{A}$. [3]
- In a transistor if $I_C = 4.9\text{mA}$ and $I_E = 5\text{mA}$, Calculate the value of α . [3]

Question 5

- A transistor can work as an amplifier, briefly describe how it works? [5]
- In a common base connection, $\alpha = 0.90$. The voltage drop across 3 kilo ohms resistance which is connected in the collector is 3V. Calculate the base current. [5]

Question 6

Define the following terms as used in the transistors:

- Thermal runaway. [2]
- Temperature dependence. [2]
- Stabilization. [2]
- Operating point. [2]

e. Stability.

[2]

Question 7

a. What is faithful amplification?

[2]

b. How is faithful amplification achieved

[3]

c. Name the conditions for faithful amplification?

[6]

Question 8

a. What is transistor biasing?

[3]

b. What is its basic purpose?

[3]

c. What is a biasing circuit?

[3]

Question 9

Give short explanations of the following terms.

a. Unipolar logic family.

[3]

b. Bipolar logic family.

[3]

c. Auxiliary Memory.

[2]

d. Main memory.

[2]

Question 10

The logic families are classified into two types: (i) Bipolar logic families, and (ii) Unipolar logic families.

a. Explain the two terms.

[4]

b. Give **three** examples of bipolar logic family.

[3]

c. Give **three** examples of unipolar logic family.

[3]